

FEE321 – E.C.T IIA – Oct 2020

Lecture 8: Laplace Transform (2) (2 hrs)

Lecturer: *Prof H A Ouma*

27/11/2020

Overview

Today's class continues the look at LT and its application

- Sample LT calculation (continued)
- Sample LT pairs
- Examples of LT application in circuit analysis

Content

- **Sample LT calculation (continued)**

Laplace transform[9]

Examples

2. Exponential function, $f(t) = e^{-at}$

$$\begin{aligned}\mathcal{L}[f(t)] &= \int_0^{\infty} f(t)e^{-st} dt = \int_0^{\infty} e^{-at} e^{-st} dt = \int_0^{\infty} e^{-(s+a)t} dt \\ &= -\frac{1}{s+a} \left\{ e^{-(s+a)t} \right\}_0^{\infty} = -\frac{1}{s+a} \left\{ e^{-(\sigma+a)t} e^{-j\omega t} \right\}_0^{\infty} \\ &= \frac{1}{s+a} \left\{ 1 - e^{-(\sigma+a)\infty} e^{-j\omega\infty} \right\}\end{aligned}$$

Exponential terms only vanish under the condition, $(\sigma + a) > 0$

$$= \frac{1}{s+a} \quad \text{ROC: } (\text{Re}[s+a] = \sigma + a) > 0$$

Thus

$$e^{-at} \Leftrightarrow \frac{1}{s+a}$$

Laplace transform[10]

Examples

3. Linear combination, $f(t) = a_1 f_1(t) + a_2 f_2(t)$

$$\begin{aligned}\mathcal{L}[f(t)] &= \int_0^{\infty} f(t)e^{-st} dt = \int_0^{\infty} \{a_1 f_1(t) + a_2 f_2(t)\} e^{-st} dt \\ &= \int_0^{\infty} \{a_1 f_1(t)\} e^{-st} dt + \int_0^{\infty} \{a_2 f_2(t)\} e^{-st} dt \\ &= a_1 \int_0^{\infty} f_1(t) e^{-st} dt + a_2 \int_0^{\infty} f_2(t) e^{-st} dt \\ &= a_1 F_1(s) + a_2 F_2(s)\end{aligned}$$

Thus $a_1 f_1(t) + a_2 f_2(t) \Rightarrow a_1 F_1(s) + a_2 F_2(s)$

Laplace transform[11]

Examples

4. Complex shift, $f_1(t) = e^{-at} f(t)$

$$\begin{aligned}\mathcal{L}[f_1(t)] &= \int_0^{\infty} f_1(t) e^{-st} dt = \int_0^{\infty} e^{-at} f(t) e^{-st} dt \\ &= \int_0^{\infty} f(t) e^{-(s+a)t} dt \\ &= F(s + a)\end{aligned}$$

Thus $e^{-at} f(t) \rightleftharpoons F(s + a)$

Laplace transform[12]

Examples

5. Real shift, $f_1(t) = f(t - t_o)u(t - t_o)$

$$\begin{aligned}\mathcal{L}[f_1(t)] &= \int_0^{\infty} f_1(t)e^{-st}dt = \int_0^{\infty} f(t - t_o)u(t - t_o)e^{-st}dt \\&= \int_{t_o}^{\infty} f(t - t_o)e^{-st}dt = \int_0^{\infty} f(\alpha)e^{-s(\alpha+t_o)}d\alpha \quad ; \text{ with } \alpha = t - t_o \\&= \int_0^{\infty} f(\alpha)e^{-\alpha s}e^{-st_o}d\alpha = e^{-st_o} \int_0^{\infty} f(\alpha)e^{-\alpha s}d\alpha \\&= e^{-st_o}F(s)\end{aligned}$$

Thus $f(t - t_o)u(t - t_o) \rightleftharpoons e^{-st_o}F(s)$

Laplace transform[13]

Examples

6. Dirac delta, $f(t) = \delta(t)$

$$\begin{aligned}\mathcal{L}[f(t)] &= \int_0^{\infty} f(t)e^{-st} dt \\ &= \int_0^{\infty} \delta(t)e^{-st} dt \\ &= \int_0^{\infty} \delta(t)e^{-s \times 0} dt \\ &= \int_0^{\infty} \delta(t) dt \\ &= 1\end{aligned}$$

Thus $\delta(t) \Rightarrow 1$

Content

- Sample LT calculation (continued)
- **Sample LT pairs**

Laplace transform[14]

Some LT pairs

$f(t), t \geq 0$	$F(s)$	ROC
$\delta(t)$	1	$\forall s$
$u(t)$	$\frac{1}{s}$	$Re(s) > 0$
t	$\frac{1}{s^2}$	$Re(s) > 0$
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$	$Re(s) > 0$
$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$	$Re(s) > 0$
$e^{-at} \cos \omega t$	$\frac{(s+a)}{(s+a)^2 + \omega^2}$	$Re(s) > -a$
$\sinh \omega t$	$\frac{\omega}{s^2 - \omega^2}$	$Re(s) > 0$
$\cosh \omega t$	$\frac{s}{s^2 - \omega^2}$	$Re(s) > 0$

Content

- Sample LT calculation (continued)
- Sample LT pairs
- **Examples of LT application in circuit analysis**

LT application[1]

Example 1

A series RL circuit is supplied from a dc source of V volts. The source is switched on at $t = 0$.

- i. Dc source switched on at $t = 0 \Rightarrow v(t) = Vu(t)$
- ii. Zero initial current before $t = 0 \Rightarrow i_L(0^+) = 0$


Circuit LDE is given by $L \frac{di(t)}{dt} + Ri(t) = Vu(t) \quad ; t > 0$

Applying LT $\mathcal{L} \left[L \frac{di(t)}{dt} + Ri(t) = Vu(t) \right]$

$$\Rightarrow \mathcal{L} \left[L \frac{di(t)}{dt} \right] + \mathcal{L}[Ri(t)] = \mathcal{L}[Vu(t)]$$

$$\Rightarrow L[sI(s) - i(0^+)] + RI(s) = \frac{V}{s} \Rightarrow I(s)\{sL + R\} = Li(0^+) + \frac{V}{s}$$

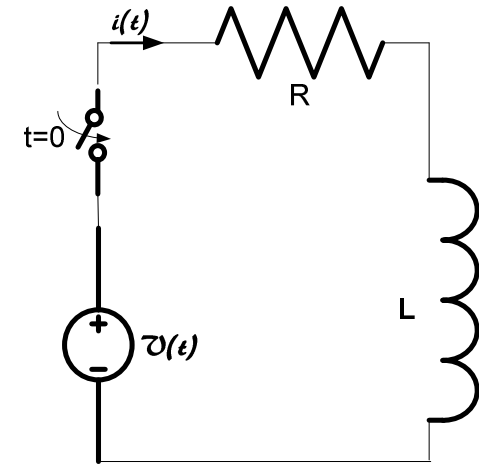Thus $I(s) = \frac{Li(0^+)}{sL + R} + \frac{V}{s(sL + R)}$



LT application[2]

Example 1 (continued)

- i. The transform equation then needs to be converted back to time domain
- ii. Partial fraction decomposition is used
- iii. Terms are organized in the forms for which LT pairs exist or LT properties may be applied

$$\Rightarrow I(s) = \frac{Li(0^+)}{sL + R} + \frac{V}{s(sL + R)} = \frac{i(0^+)}{s + \frac{R}{L}} + \frac{\frac{V}{L}}{s(s + \frac{R}{L})} = I_1(s) + I_2(s)$$

$$\text{Since } e^{-at} \Leftrightarrow \frac{1}{s + a} \quad \Rightarrow \quad I_1(s) = \frac{i(0^+)}{s + \frac{R}{L}} \Leftrightarrow i_1(t) = i(0^+)e^{-\frac{R}{L}t}$$

Using partial fraction decomposition for the second term

$$I_2(s) = \frac{\frac{V}{L}}{s(s + \frac{R}{L})} = \frac{A}{s} + \frac{B}{s + \frac{R}{L}} \quad \Rightarrow \quad A = s \left(\frac{\frac{V}{L}}{s(s + \frac{R}{L})} \right) \Big|_{s=0} = \frac{V}{R}$$

.

$$\Rightarrow B = \left(s + \frac{R}{L} \right) \left(\frac{\frac{V}{L}}{s(s + \frac{R}{L})} \right) \Big|_{s=-\frac{R}{L}} = -\frac{V}{R}$$

LT application[3]

Example 1 (continued)

$$\begin{aligned}\therefore I_2(s) &= \frac{\frac{V}{L}}{s(s + \frac{R}{L})} = \frac{\frac{V}{R}}{s} - \frac{\frac{V}{R}}{s + \frac{R}{L}} \Rightarrow i_2(t) = \frac{V}{R} \left(u(t) - e^{-\frac{R}{L}t} \right) \\ \Rightarrow I(s) &= \frac{i(0^+)}{s + \frac{R}{L}} + \frac{\frac{V}{R}}{s} - \frac{\frac{V}{R}}{s + \frac{R}{L}} \Rightarrow i(t) = u(t) \left\{ i(0^+) e^{-\frac{R}{L}t} + \frac{V}{R} \left(u(t) - e^{-\frac{R}{L}t} \right) \right\}\end{aligned}$$

Expression may be re-arranged thus

$$i(t) = u(t) \left\{ \frac{V}{R} u(t) + \left[i(0^+) - \frac{V}{R} \right] e^{-\frac{R}{L}t} \right\} \text{ A}$$

The first term in the curly brackets is the **steady state** circuit current

The second term in the curly brackets is the **transient** circuit current

NB: At steady state, for dc excitation the inductor appears as a **short circuit**

The unit step MUST always be included in these LT solutions as $t > 0$ is a condition for LT

If the zero initial conditions are applied $i(t) = u(t) \left\{ \frac{V}{R} \left(u(t) - e^{-\frac{R}{L}t} \right) \right\} \text{ A}$

LT application[4]

Example 1b (Numerical)

A series RL circuit is supplied from a dc source of 20 volts. The source is switched on at $t = 0$. There is zero initial current in the circuit. Let $R = 5\Omega$, and $L = 0.5H$

Circuit LDE as before is given by
$$L \frac{di(t)}{dt} + Ri(t) = Vu(t) \quad ; t > 0$$

Substituting values $0.5 \frac{di(t)}{dt} + 5i(t) = 20u(t) \quad ; t > 0$


Applying LT $\mathcal{L} \left[0.5 \frac{di(t)}{dt} + 5i(t) = 20u(t) \right]$

$$\Rightarrow 0.5[sI(s) - i(0^+)] + 5I(s) = \frac{20}{s} \Rightarrow I(s)\{0.5s + 5\} = 0.5i(0^+) + \frac{20}{s}$$

$$\text{Thus } I(s) = \frac{0.5i(0^+)}{0.5s + 5} + \frac{20}{s(0.5s + 5)} = \frac{i(0^+)}{s + 10} + \frac{40}{s(s + 10)} = I_1(s) + I_2(s)$$

The first term $I_1(s)$ is of a form we recognize and can immediately be inverted. The second term $I_2(s)$ needs to be decomposed into two fractions
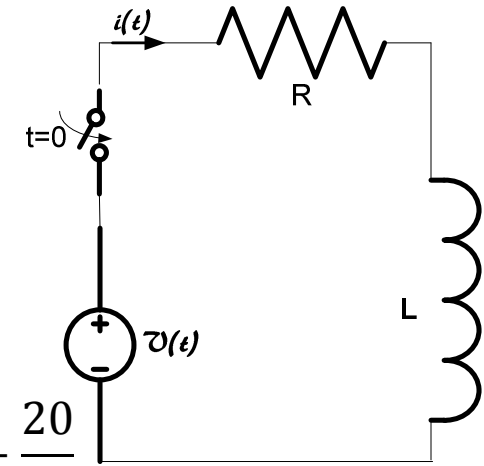
$$I_2(s) = \frac{40}{s(s + 10)} = \frac{A}{s} + \frac{B}{s + 10}$$



LT application[5]

Example 1b (continued) $I_2(s) = \frac{40}{s(s+10)} = \frac{A}{s} + \frac{B}{s+10}$

$$\Rightarrow A = s \left(\frac{40}{s(s+10)} \right) \Big|_{s=0} = 4 \quad \text{and} \quad B = (s+10) \left(\frac{40}{s(s+10)} \right) \Big|_{s=-10} = -4$$

$$I_2(s) = \frac{40}{s(s+10)} = \frac{4}{s} - \frac{4}{s+10} \quad \text{and} \quad I(s) = \frac{4}{s} - \frac{\{4 - i(0^+)\}}{s+10}$$

$$e^{-at} \Leftrightarrow \frac{1}{s+a} \quad \text{and} \quad u(t) \Leftrightarrow \frac{1}{s}$$

$$i(t) = u(t)\{4u(t) - [4 - i(0^+)]e^{-10t}\} \quad A$$

.

Note the **steady state** component and the **transient** component

.

LT application[6]

Example 2

A series RC circuit is supplied from a dc source of V volts. The source is switched on at $t = 0$. Assume there is zero voltage across the capacitor at $t = 0$

- i. Dc source switched on at $t = 0 \Rightarrow v(t) = Vu(t)$
- ii. Zero initial voltage $\Rightarrow v_C(0^+) = 0$

Circuit LDE is given by $\frac{1}{C} \int_{-\infty}^t i(t) dt + Ri(t) = Vu(t) \quad ; t > 0$

Applying LT $\mathcal{L} \left[\frac{1}{C} \int_{-\infty}^t i(t) dt + Ri(t) = Vu(t) \right]$


$$\Rightarrow \mathcal{L} \left[\frac{1}{C} \int_{-\infty}^0 i(t) dt + \frac{1}{C} \int_0^t i(t) dt \right] + \mathcal{L}[Ri(t)] = \mathcal{L}[Vu(t)]$$

$$\Rightarrow \mathcal{L} \left[v_C(0^+) + \frac{1}{C} \int_0^t i(t) dt \right] + \mathcal{L}[Ri(t)] = \mathcal{L}[Vu(t)]$$

$$\Rightarrow \frac{v_C(0^+)}{s} + \frac{I(s)}{sC} + RI(s) = \frac{V}{s} \quad \Rightarrow I(s) \left\{ \frac{1}{sC} + R \right\} = \frac{V - v_C(0^+)}{s}$$

Thus
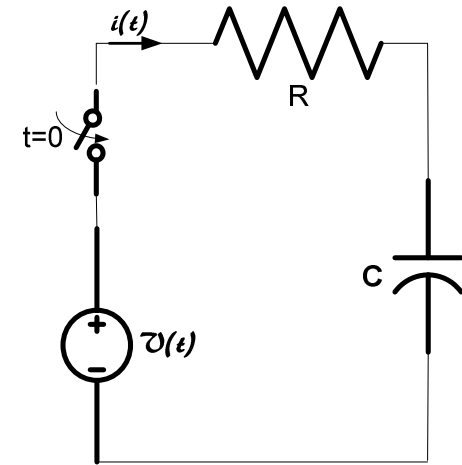
$$\Rightarrow I(s) = \frac{sC(V - v_C(0^+))}{s(sCR + 1)}$$



LT application[7]

Example 2 (continued)

- i. The transform equation then needs to be converted back to time domain
- ii. Partial fraction decomposition not needed this time
- iii. Let us first assume the initial conditions were not zero, to see complete solution
- iv. Terms are organized in the forms for which LT pairs exist or LT properties may be applied

$$I(s) = \frac{C(V - v_C(0^+))}{sCR + 1} = \frac{\frac{1}{R}(V - v_C(0^+))}{s + \frac{1}{CR}}$$

$$\text{Since } e^{-at} \Leftrightarrow \frac{1}{s + a} \Rightarrow \frac{\frac{1}{R}(V - v_C(0^+))}{s + \frac{1}{CR}} \Leftrightarrow \frac{1}{R}(V - v_C(0^+))e^{-\frac{1}{CR}t}$$

$$\text{The current is therefore } i(t) = u(t) \left\{ \frac{1}{R}(V - v_C(0^+))e^{-\frac{1}{CR}t} \right\} A$$

- Only **transient** current exists
- Makes sense because in **steady state** the capacitor appears as an **open circuit** under dc excitation, and no current flows
- Again the multiplication by $u(t)$ is mandatory due to definition of LT

$$\text{For zero initial conditions } i(t) = \frac{Vu(t)}{R} e^{-\frac{1}{CR}t} A$$

LT application[8]

Example 2b (numerical)


A series RC circuit is supplied from a dc source of 20 volts. The source is switched on at $t = 0$. There is zero voltage across the capacitor at $t = 0$. Let $R = 5\Omega$, and $C = 0.1F$

Circuit LDE is given by $\frac{1}{C} \int_{-\infty}^t i(t) dt + Ri(t) = Vu(t) \quad ; t > 0$

Substituting and applying LT $\mathcal{L} \left[10 \int_{-\infty}^t i(t) dt + 5i(t) = 20u(t) \right]$

$$\Rightarrow \mathcal{L} \left[10 \int_{-\infty}^0 i(t) dt + 10 \int_0^t i(t) dt \right] + \mathcal{L}[5i(t)] = \mathcal{L}[20u(t)]$$
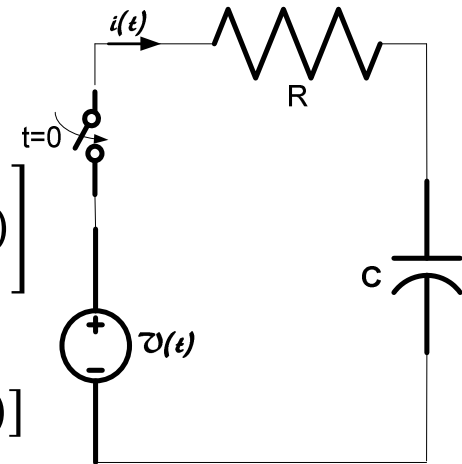
$$\Rightarrow \mathcal{L} \left[v_C(0^+) + 10 \int_0^t i(t) dt \right] + \mathcal{L}[5i(t)] = \mathcal{L}[20u(t)]$$



LT application[9]

Example 2b (numerical)

Thus

$$\Rightarrow \frac{v_C(0^+)}{s} + \frac{10I(s)}{s} + 5I(s) = \frac{20}{s} \quad \Rightarrow I(s) \left\{ \frac{1}{0.1s} + 5 \right\} = \frac{20 - v_C(0^+)}{s}$$
$$\Rightarrow I(s) = \frac{0.1s(20 - v_C(0^+))}{s(0.5s + 1)} = \frac{0.2(20 - v_C(0^+))}{s + 2} = \frac{(4 - 0.2v_C(0^+))}{s + 2}$$

This form is easily recognized and is easily inverted to give

$$i(t) = u(t)\{4 - 0.2v_C(0^+)\}e^{-2t} \quad A$$

As before it is noted that only the **transient component** exists in this response

.

Summary

Today's class looked at Laplace transform and application

- Sample LT calculation (continued)
- Sample LT pairs
- Examples of LT application in circuit analysis

QUESTIONS?